

EC 447 ACTIVE FILTERS
COURSE PROJECT REPORT

REALIZATION OF 4TH ORDER LOW PASS FILTER USING Gm - C

Submitted by


Jupudi Vasavi 191EC121

Hemadarshini Gopal 191EE217

VII semester B.Tech ECE

Under the guidance of

Prof. Laxminidhi T

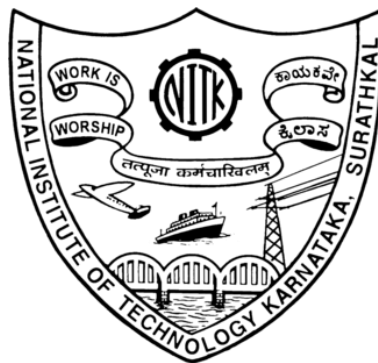

Department of Electronics and Communication Engineering,
National Institute of Technology, Surathkal

November 2022

▪ **AIM**

Design a Transconductance-C (Gm-C) low pass filter in 0.35 μm CMOS technology node from TSMC using LTSpice circuit simulator (or any other suitable circuit simulator) for the specifications mentioned.

▪ **BROAD EXPECTATIONS:**

Realizing an ideal Gm-C Filters

1. a) Ideal Filer using RLC circuit which meets the specifications
 b) Ideal Gm-C filter for the specifications using macromodel for the Gm.
2. Designing the transconductor in 0.35 μm CMOS technology node from TSMC and validating its use as a Gm-C integrator.

The capacitor calculated to be used in the first node of the filter may be used as the integrating capacitor for testing the Gm-C integrator.

3. Realize the transistor level Gm-C filter for the given specification.

▪ **COMMON SPECIFICATIONS:**

1. Fourth order Maximally flat response
2. Power supply 3.3 V
3. Use length of 0.5 μm for all transistors
4. Use even number of fingers for the transistors.

▪ **TRANSCONDUCTOR SPECIFICATIONS:**

1. Gm = 1 mS
2. Gate overdrive for input transistors = 200 mV
3. Input/output common-mode voltage = 1.65 V

▪ **FILTER SPECIFICATIONS:**

1. Attenuation at pass band edge = 2 dB
2. Band-edge = 110 MHz

■ METHODOLOGY:

- a. Ideal filter realization using RLC which meet the specifications.
- I. Initially fourth order prototype Butterworth filter is designed and verified using LT Spice.

Design:

a. Ideal Filter using RLC circuit.

Given: pass band attenuation = 2 dB
Band edge = 110 MHz
order, n = 4.

$\omega_{p, \text{int}} = 110 \text{ MHz} \times 2\pi$, pass band edge for maximally flat response

$\omega_{p, b} \rightarrow$ pass band edge for butterworth filter.

\rightarrow Finding the value of ϵ

$$-20 \log |T_n(j\omega)| = 2$$

$$\Rightarrow -20 \log \left(\frac{1}{\sqrt{1+\epsilon^2}} \right) = 2$$

$$\Rightarrow 1 + \epsilon^2 = 10^{0.2}$$

$$\Rightarrow \boxed{\epsilon = 0.7647}$$

$$\rightarrow Q_1 = \frac{1}{2 \cos(22.5)} = 0.5411$$

$$Q_2 = \frac{1}{2 \cos(67.5)} = 1.3065$$

\rightarrow Transfer function of a 4th order prototype Butterworth filter =

$$\frac{1}{\left(s^2 + \frac{1}{Q_1}s + 1\right)\left(s^2 + \frac{1}{Q_2}s + 1\right)}$$

$$= \frac{1}{\left(s^2 + \frac{1}{0.541}s + 1\right)\left(s^2 + \frac{1}{1.3065}s + 1\right)}$$

→ For maximally flat response filter

$$\left|T_n(j\omega)\right|_{mf}^2 = \frac{1}{1 + \epsilon^2 \omega^{2n}}$$

For butterworth

$$\left|T_n(j\omega)\right|^2 = \frac{1}{1 + \omega^{2n}}$$

For any pass band edge $\omega_{p,B}$,

$$\left|T_n(j\omega)\right|_{\omega_{p,mf}} = \left|T_n(j\omega)\right|_{\omega_{p,B}}$$

$$\left(\frac{\omega}{\omega_{p,mf}}\right)^{2n} \epsilon^2 = \left(\frac{\omega}{\omega_{p,B}}\right)^{2n}$$

$$\Rightarrow \boxed{\omega_{p,B} = \epsilon^{-1/n} \omega_{p,mf}} \Rightarrow \omega_{p,B} = (0.7647)^{-0.25} \times (110 \times 10^6 \times 2\pi) = 739.095 \text{ Mrad/sec}$$

→ Finding the values of L_1, C_1, L_2, C_2 .

$$R_1 = R_2 = 1 \text{ K}\Omega$$

$$Q_1 = \frac{1}{R_1} \sqrt{\frac{L_1}{C_1}} \quad \text{--- (1) and } \omega_p = \frac{1}{\sqrt{L_1 C_1}} \quad \text{--- (2)}$$

Multiplying (1) and (2)

$$\Rightarrow Q_1 \omega_{p,b} = \frac{1}{R_1 C_1} \Rightarrow C_1 = \frac{1}{Q_1 \omega_{p,b} R_1}$$

$$= \frac{1}{0.541 \times 739.095 \times 10^6 \times 10^3} = \underline{\underline{2.5 \text{ pF}}}$$

$$L_1 = Q_1^2 R_1^2 C_1$$

$$= (0.541)^2 \times (10^3)^2 \times 2.5 \times 10^{-12}$$

$$L_1 = 0.731 \mu H$$

Similarly,

$$C_2 = \frac{1}{Q_2^2 \omega_b^2 R_2}$$

$$= \frac{1}{1.3065 \times 739.095 \times 10^6 \times 10^3}$$

$$= 1.0355 pF$$

$$L_2 = 1.0355 \times 10^{-12} \times (1.3065)^2 \times (10^3)^2$$

$$= 1.767 \mu H$$

$$\therefore R_1 = 1 k\Omega$$

$$R_2 = 1 k\Omega$$


$$L_1 = 0.731 \mu H$$

$$L_2 = 1.767 \mu H$$


$$C_1 = 2.5 pF$$

$$C_2 = 1.0355 pF$$

Circuit: (Prototype)

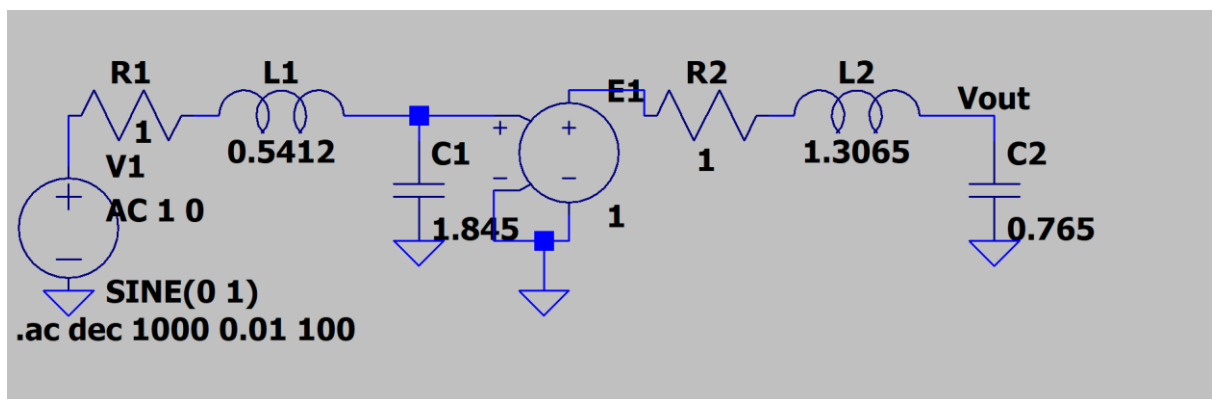


Waveforms:

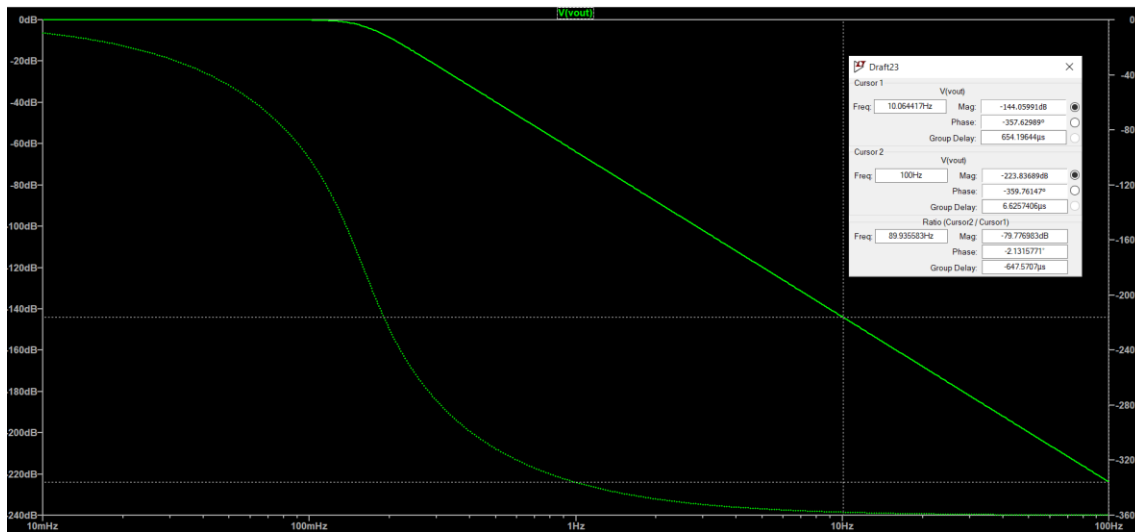


- II. For the given Maximally flat response, corresponding Butterworth pass band edge has been found out.
- III. Using the new butterworth pass band edge and given transconductance $G_m=1\text{mS}$, R_1 , L_1 , C_1 and R_2 , C_2 , L_2 are calculated.


Circuit:

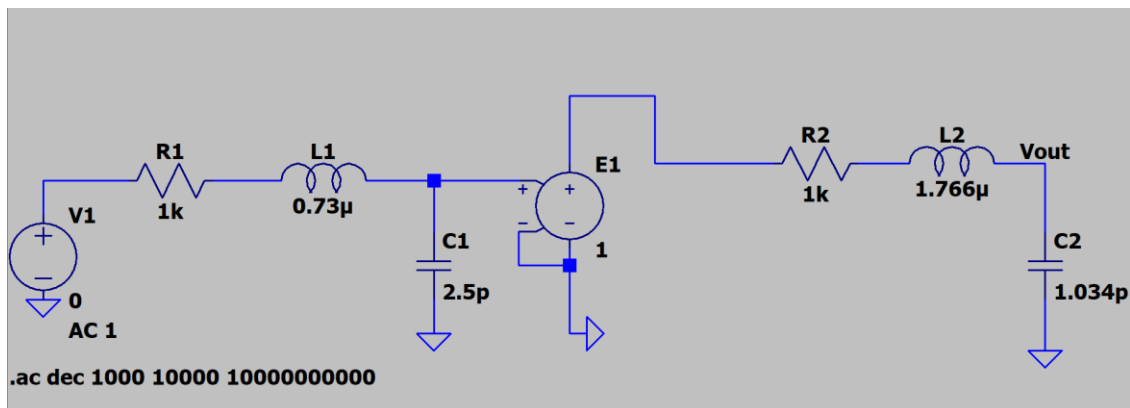

Waveforms:

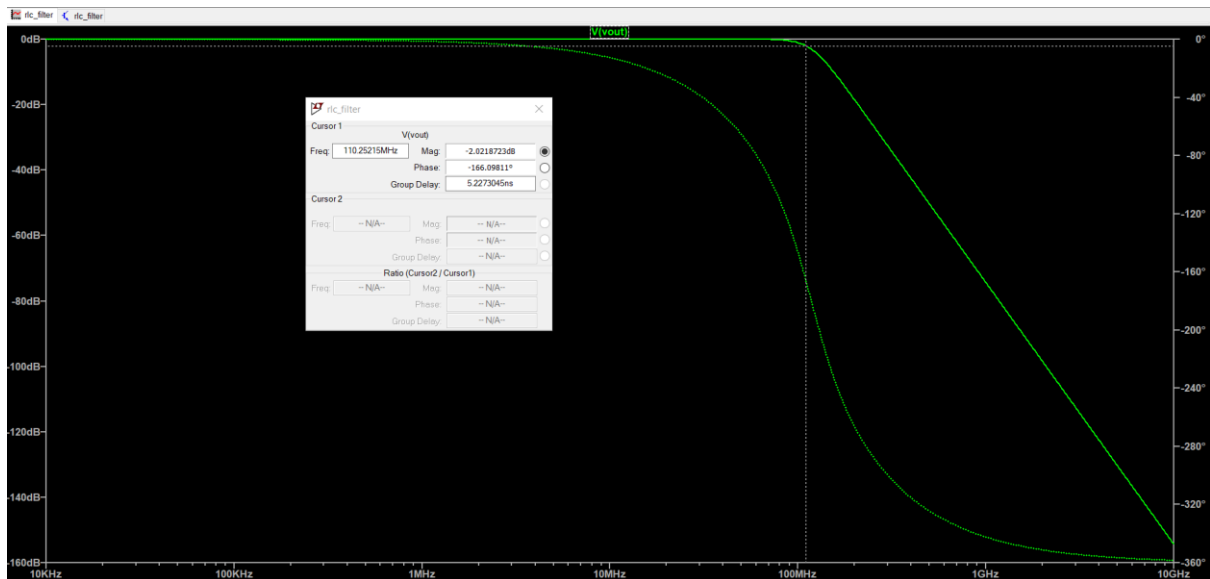

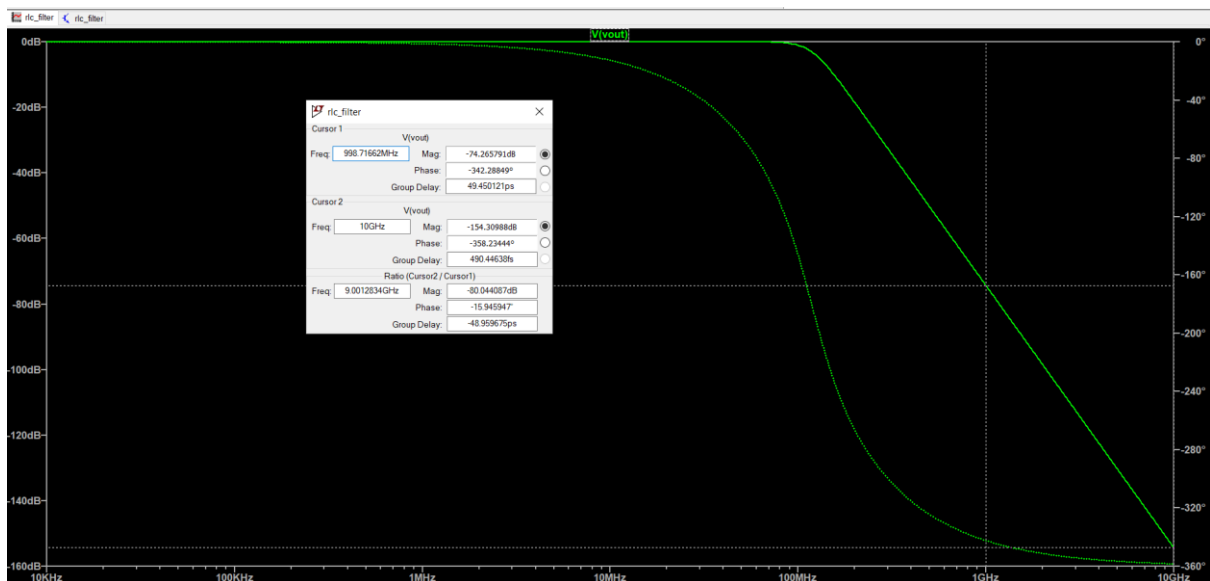From the graph,
At frequency 110 MHz, Gain obtained = **-2.02dB** (Attenuation=2 dB)



From the Graph,
Roll-off obtained at $\omega_p = 110 \text{ MHz}$ is **-80.044087** which is equal to the roll-off of a 4th butterworth response $-20 \times 4 = -80$

b) Ideal Gm-C filter for the specifications using macromodel for the Gm.

I. As 4th order Butterworth Low Pass Filter is obtained by cascading 2 second order low pass filters, each 2nd low pass filter is obtained using Gm and C and are cascaded directly without any buffer as there is no loading effect.

Design:

b Given: $G_m = 1 \text{ mS}$


We know that $L = \frac{C}{g_m^2}$

$$\omega_0 = \frac{1}{\sqrt{LC_1}}$$

$$\omega_0 = \frac{1}{\sqrt{\frac{C_2}{g_m^2} \times C_1}}$$

$$\Rightarrow \omega_0 = \frac{g_m}{\sqrt{C_1 C_2}}$$

$$Q = \frac{R}{\frac{L}{C}} = \frac{1}{g_m} \times \frac{C_2}{\sqrt{\frac{C_2}{g_m^2} \times C_1 + 1}}$$
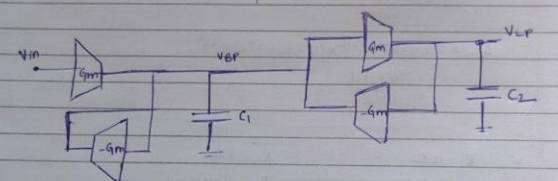
$$\Rightarrow Q = \sqrt{\frac{C_1}{C_2}}$$


For the 2nd order filter with quality factor as Q_1 , the capacitor values are C_1 and C_2 .

$$\Rightarrow \omega_0 Q_1 = \frac{g_m}{C_2}$$

$$\Rightarrow C_2 = \frac{g_m}{\omega_0 Q_1} = \frac{1 \times 10^{-3}}{739.095 \times 10^6 \times 0.541}$$

$$C_2 = 2.5 \text{ pF}$$

$$\Rightarrow C_1 = Q_1^2 C_2 = 0.73 \text{ pF}$$

For the 2nd order filter with Quality factor as Q_2 , the capacitor values are C_3 and C_4 .

$$\Rightarrow \omega_0 Q_2 = \frac{g_m}{C_4}$$

$$\Rightarrow C_4 = \frac{1 \times 10^{-3}}{739.095 \times 10^6 \times 1.3065}$$

$$= 1.035 \text{ pF}$$

$$\Rightarrow C_3 = Q_2^2 C_4$$


$$= (1.3065)^2 \times 1.035 \times 10^{-12}$$

$$= 1.767 \text{ pF}$$


$$\therefore C_1 = 0.73 \text{ pF} \quad C_3 = 1.767 \text{ pF}$$

$$C_2 = 2.5 \text{ pF} \quad C_4 = 1.035 \text{ pF}$$


Circuit:

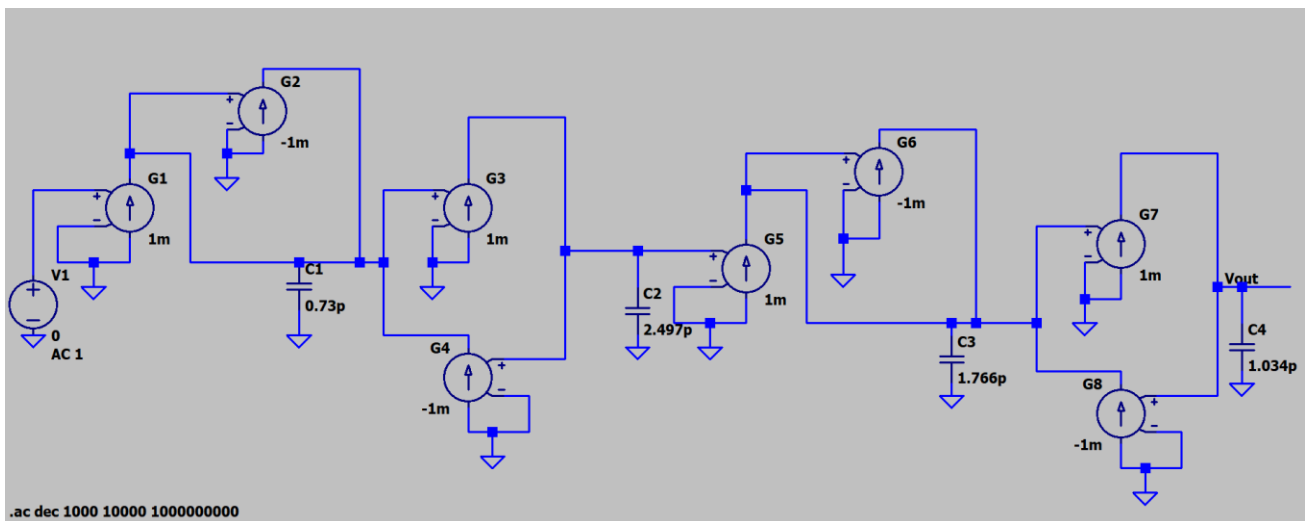

Waveforms:

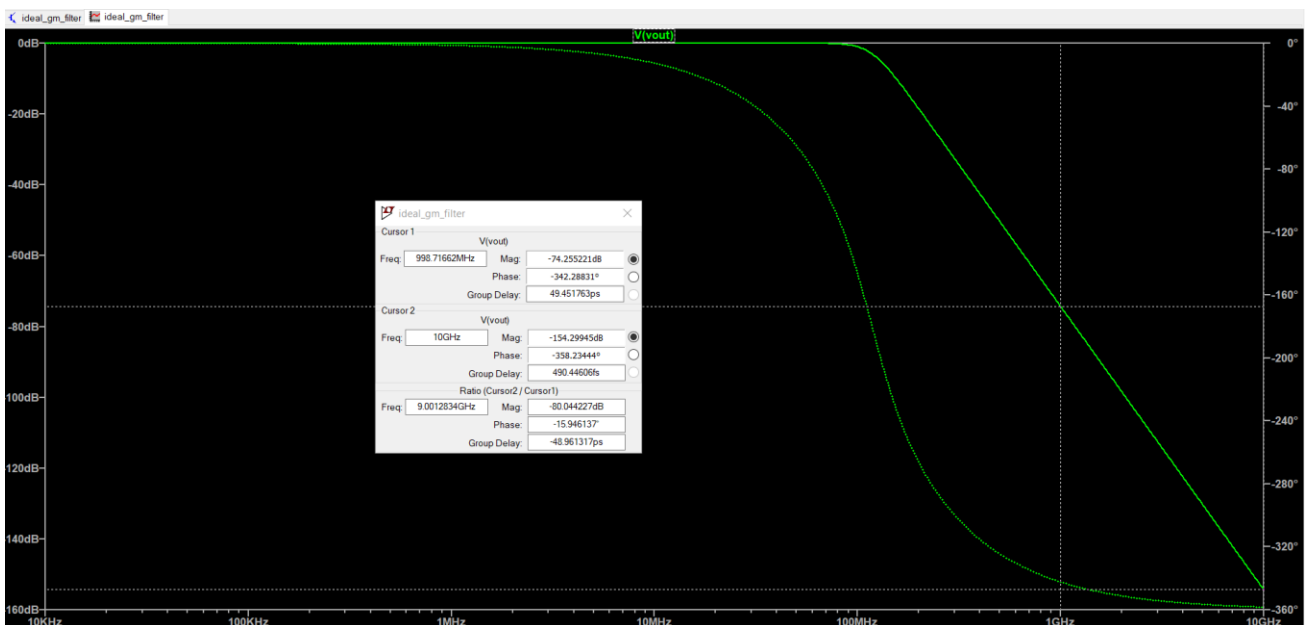

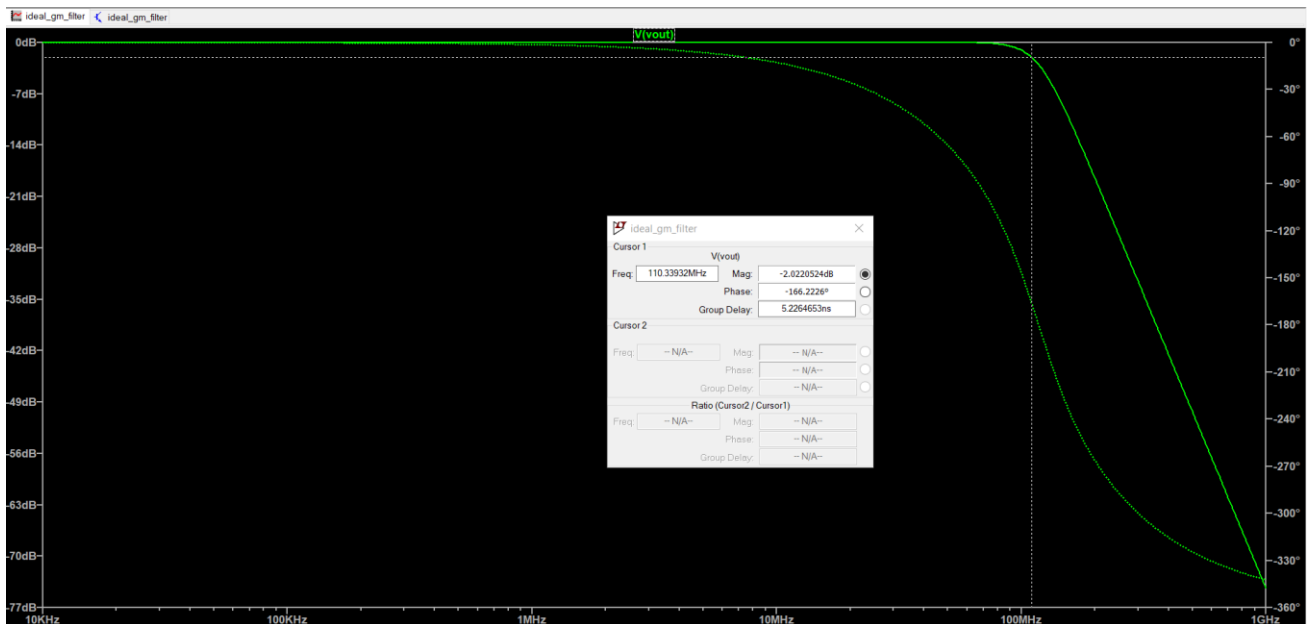From the graph,
Gain at $\omega_p = 110\text{MHz}$ is -2.0220524dB (Attenuation $\approx 2\text{dB}$ approximately)



From the graph,


Roll-off measured in between 1GHz and 10GHz is -80.0442 which is equal to the roll-off of a 4th butterworth response $-20 \times 4 = -80\text{dB}$.

2. Designing the transconductor in 0.35 μm CMOS technology node from TSMC and validating its use as a Gm-C integrator.

Transconductance = 1 mS

$V_{ds,sat}$ = 200 mV

NMOS Specifications tuned:

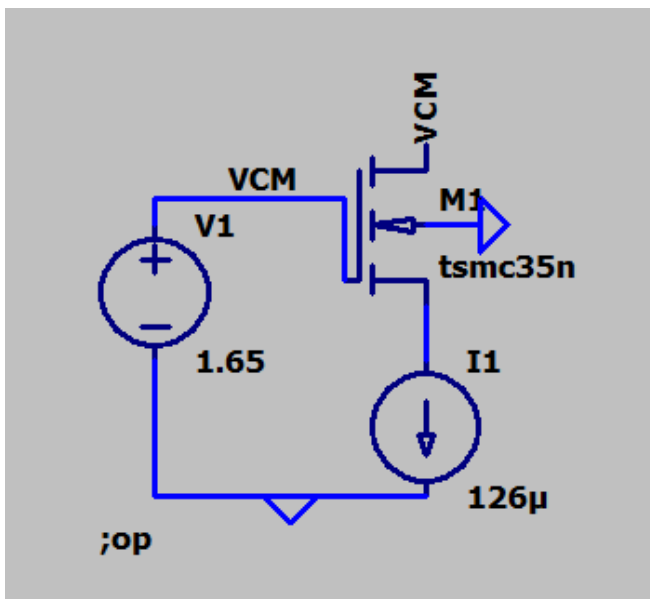

Monolithic MOSFET - M1

Model Name:	tsmc35n	OK
Length(L):	0.5u	Cancel
Width(W):	1.8u	
Drain Area(AD):		
Source Area(AS):		
Drain Perimeter(PD):		
Source Perimeter(PS):		
No. Parallel Devices(M):	8	

tsmc35n l=0.5u w=1.8u m=8

PMOS specifications obtained:

Monolithic MOSFET - M5

Model Name: tsmc35p OK

Length(L): 0.5u Cancel

Width(W): 1.8u

Drain Area(AD):

Source Area(AS):


Drain Perimeter(PD):

Source Perimeter(PS):

No. Parallel Devices(M): 20

tsmc35p l=0.5u w=1.8u m=20

Circuit:

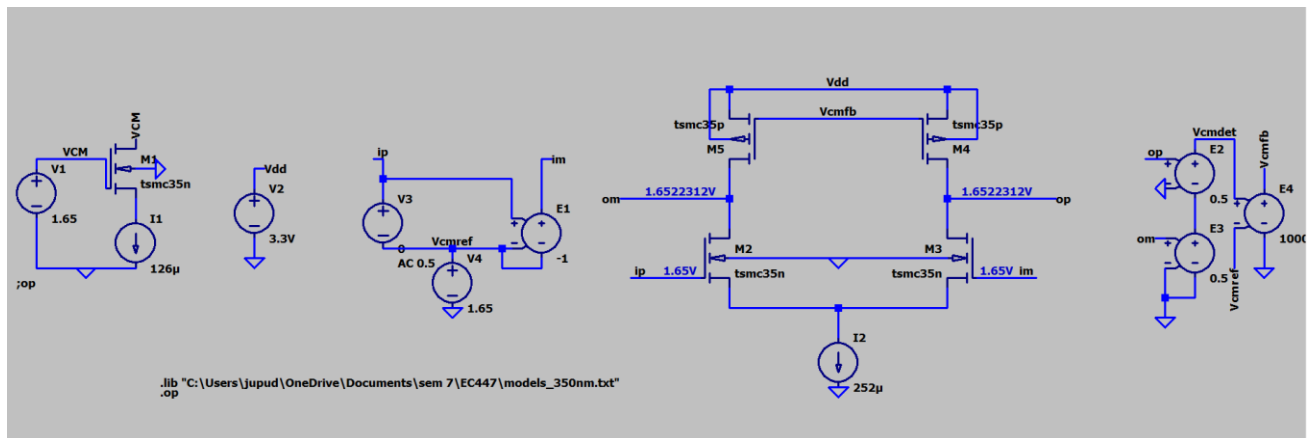

SPICE Error Log Results:

SPICE Error Log: C:\Users\jupud\OneDrive\Documents\sem 7\EC447\gm_macro.log

Circuit: * C:\Users\jupud\OneDrive\Documents\sem 7\EC447\gm_macro.asc


Ignoring BSIM parameter XL
 Ignoring BSIM parameter XW
 Ignoring BSIM parameter XL
 Ignoring BSIM parameter XW
 Warning: Pd = 0 is less than W.
 Warning: Ps = 0 is less than W.
 Warning: Pd = 0 is less than W.
 Warning: Ps = 0 is less than W.
 Direct Newton iteration for .op point succeeded.
 Semiconductor Device Operating Points:

Name:	m5	m4	m3	m2	m1
Model:	tsmc35p	tsmc35p	tsmc35n	tsmc35n	tsmc35n
Id:	-1.26e-04	-1.26e-04	1.26e-04	1.26e-04	1.26e-04
Vgs:	-1.07e+00	-1.07e+00	1.09e+00	1.09e+00	1.09e+00
Vds:	-1.65e+00	-1.65e+00	1.09e+00	1.09e+00	1.09e+00
Vbs:	0.00e+00	0.00e+00	-5.60e-01	-5.60e-01	-5.60e-01
Vth:	-8.05e-01	-8.05e-01	8.40e-01	8.40e-01	8.40e-01
Vdsat:	-2.39e-01	-2.39e-01	2.02e-01	2.02e-01	2.02e-01
Gm:	8.18e-04	8.18e-04	1.00e-03	1.00e-03	1.00e-03
Gds:	1.46e-05	1.46e-05	1.58e-05	1.58e-05	1.58e-05
Gmb:	1.65e-04	1.65e-04	2.14e-04	2.14e-04	2.14e-04
Cbd:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cbs:	0.00e+00	0.00e+00	0.00e+00	0.00e+00	0.00e+00
Cgsov:	6.46e-15	6.46e-15	3.37e-15	3.37e-15	3.37e-15
Cgdov:	6.46e-15	6.46e-15	3.37e-15	3.37e-15	3.37e-15
Cgbv:	1.00e-15	1.00e-15	3.63e-16	3.63e-16	3.63e-16

Required values of V_{dsat} and G_m are obtained by tuning W , number of fingers and Current value in the current source and the functioning of G_m -C integrator is verified.


- 4th-order Low Pass Butterworth Filter realization using G_m implemented in the previous step:

Circuit:

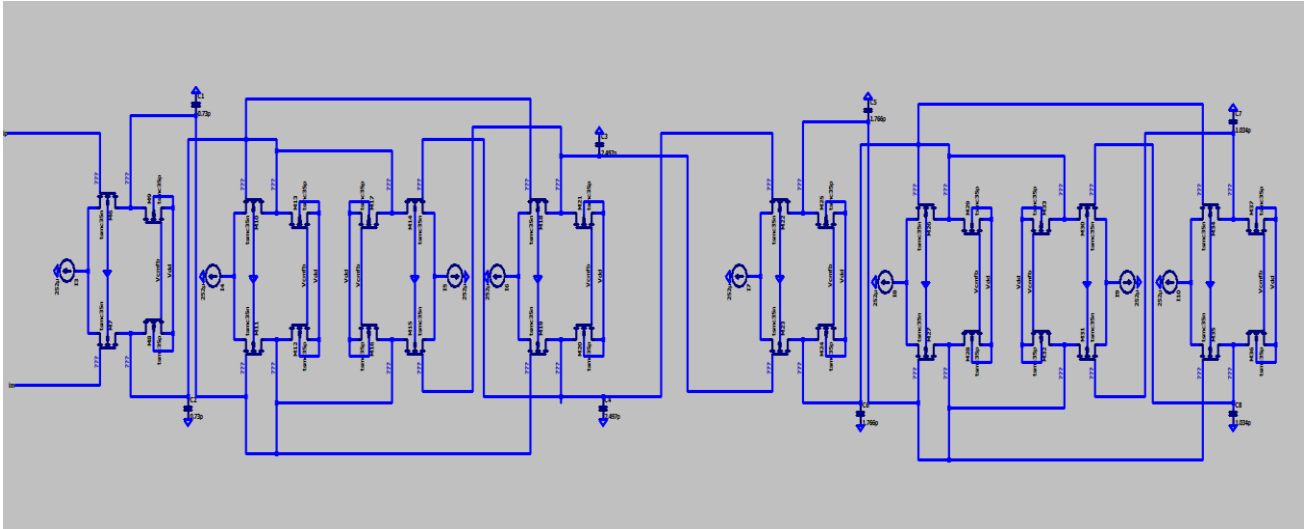

Waveforms:

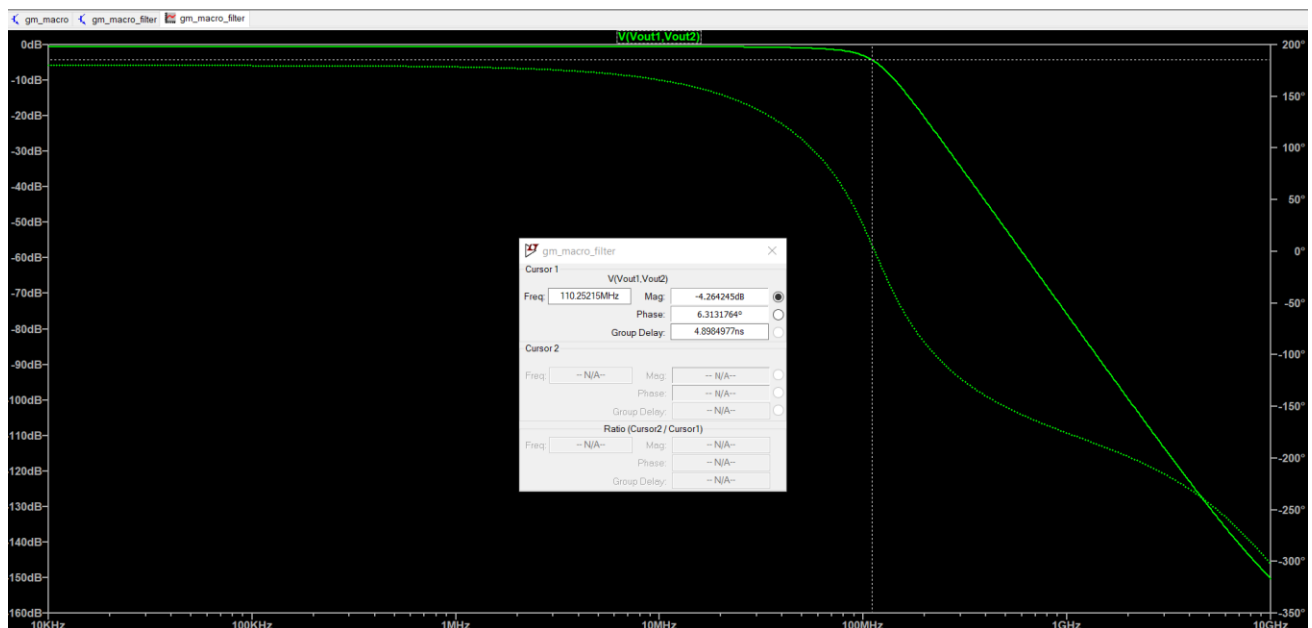The input given is differential input, so the differential voltage is measured across the output.



From the graph,

Gain obtained at pass band edge=**-4.264245dB**.

DC Gain obtained= **-565.58289m dB**.

There is a slight deviation than the required gain which is due to non-idealities like parasitic capacitances and output resistances of all the transconductors.
